

# ECE385

## Experiment #5

### An 8-Bit Multiplier in System Verilog

Chengting Yu, 3170111707

Yangkai Du, 3170112258

#### 1. Introduction

In this experiment, we build an 2's Complement 8-bit Multiplier unit, which can support two 8-bit 2's compliment numbers multiplication.

#### 2. Pre-lab question

Function	X	A	B	M	Comments for the next step
Clear A, LoadB	0	0000 0000	0000 0111	1	Since M = 1, multiplicand (available from switches S) will be added to A.
ADD	1	1100 0101	0000 0111	1	Shift XAB by one bit after ADD complete
SHIFT	1	1110 0010	1000 0011	1	Add S to A since M = 1.
ADD	1	1010 0111	1000 0011	1	Shift XAB by one bit after ADD complete
SHIFT	1	1101 0011	1100 0001	1	Add S to A since M = 1.
ADD	1	1001 1000	1100 0001	1	Shift XAB by one bit after ADD complete
SHIFT	1	1100 1100	0110 0000	0	Do not add S to A since M = 0. Shift XAB.
SHIFT	1	1110 0110	0011 0000	0	Do not add S to A since M = 0. Shift XAB.
SHIFT	1	1111 0011	0001 1000	0	Do not add S to A since M = 0. Shift XAB.
SHIFT	1	1111 1001	1000 1100	0	Do not add S to A since M = 0. Shift XAB.
SHIFT	1	1111 1100	1100 0110	0	Do not SUB S to A since M = 0. Shift XAB.
SHIFT	1	1111 1110	0110 0011	0	8th shift done. Stop. 16-bit Product in AB.


#### 3. Written description and diagrams of multiplier circuit

##### a. Summary of operation


**Operands Loading:** First store the Multiplier in S and press ClearA\_LoadB, the Multiplier in S would be loaded to Register B and Register A and DFF X would be clear to 0; then store the Multiplicand in S.

**Computing:** User need to press "Run" after "ClearA\_LoadB" is excuted, then the "add-shift" algorithm will be executed to compute the results. There are two states, add states and shift states. In add states, if  $M = B[0]$  is 0, then we do not need to accumulate the Multiplicand, just transfer to shift states. If  $M = B[0]$  is 1, then we need to accumulate the Multiplicand,  $A \leftarrow S + A$ , the sign extention bit is stored in X, then we would transfer to shift state. In shift state,  $A[0] \rightarrow B[7]$ ,  $X \rightarrow A[7]$ , every bit is shited right in Reg A and B. There would be 8 shift and 8 add/sub operation for 8 bit multiplier.

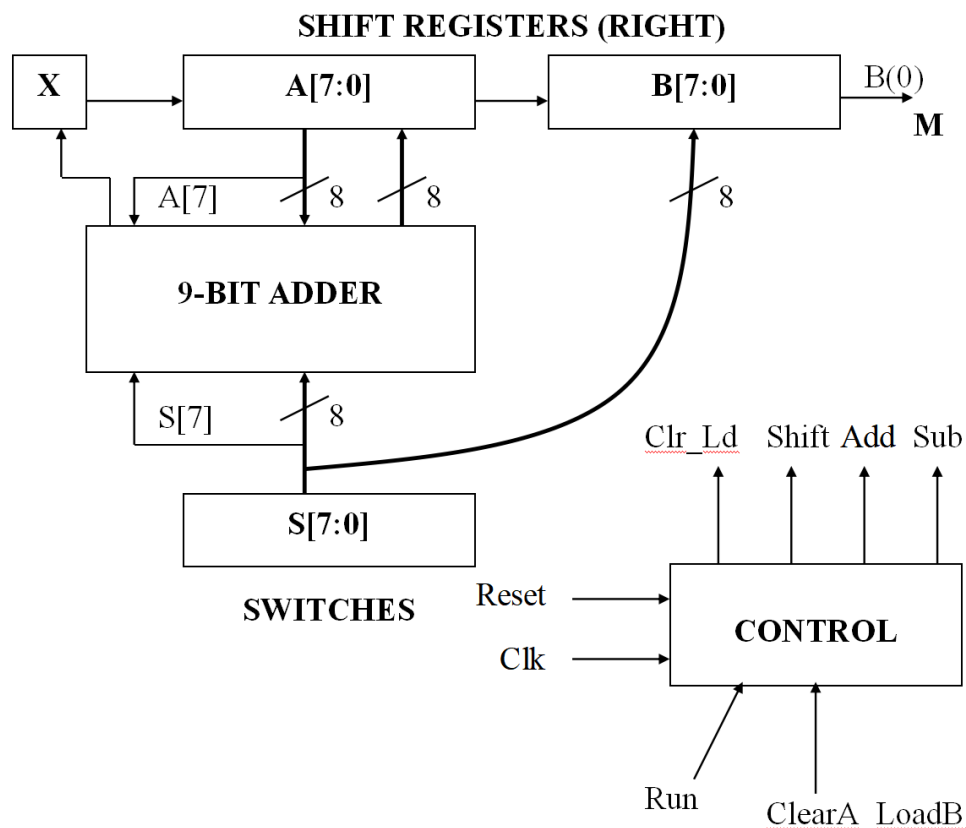**Results Store:** The final results R is 16-bit,  $R[15:8]$  is stored in Reg A, and  $R[7:0]$  is stored in Reg B.



## b. Top Level Block Diagram

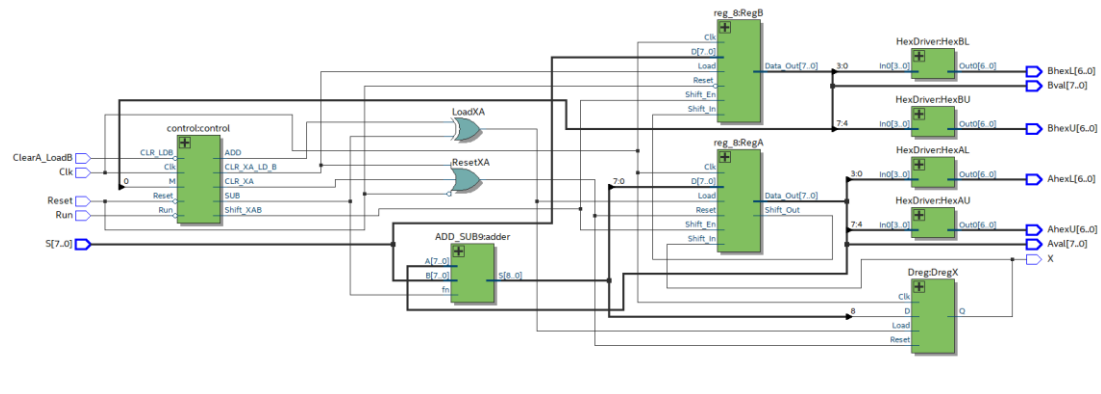

### c. Written Description of .sv Modules

```

module lab5_top1level
(
    input    logic[7:0] S,
    input    logic Clk, Reset, Run, ClearA_LoadB,
    output   logic[6:0] AhexU, AhexL, BhexU, BhexL,
    output   logic[7:0] Aval, Bval,
    output   logic X
);

    //local logic variables go here
    // logic Reset_SH, LoadA_SH, LoadB_SH, Execute_SH;
    // logic Ld_A, Ld_B, newA, newB, opA, opB, bitA, bitB, Shift_En, F_A_B;
    // logic [7:0] A, B, Din_S;
    logic[7:0] A, B;
    logic X0; // output of X
    logic XI; // input of X for next state
    logic SUB, ADD;
    logic LoadXA, ResetXA;
    logic shift;
    logic A0;
    logic fn;
    logic[8:0] ADDER_OUT;
    logic CLR_XA_LD_B;
    logic NotReset;
    logic NotRun;
    logic NotClearA_LoadB;
    logic CLR_XA;

    //We can use the "assign" statement to do simple combinational logic
    assign LoadXA = SUB ^ ADD;
    assign ResetXA = NotReset | CLR_XA_LD_B | CLR_XA;
    assign fn = SUB;
    assign XI = ADDER_OUT[8];
    assign NotReset = ~Reset;
    assign NotRun = ~Run;
    assign NotClearA_LoadB = ~ClearA_LoadB;

    //output
    assign X = X0;
    assign Aval = A;
    assign Bval = B;

    input Clk, Load, Reset, D,
    output logic Q
    Dreg DregX (.Clk(Clk), .Load(LoadXA), .Reset(ResetXA), .D(XI), .Q(X0));

    input logic Clk, Reset, Shift_In, Load, Shift_En,
    input logic [7:0] D,
    output logic Shift_Out,
    output logic [7:0] Data_Out;
    reg_8 RegA(.Clk(Clk), .Reset(ResetXA), .Shift_In(X0), .Load(LoadXA), .Shift_En(shift), .D(ADDER_OUT[7:0]), .Shift_Out(A0),
    reg_8 RegB(.Clk(Clk), .Reset(NotReset), .Shift_In(A0), .Load(CLR_XA_LD_B), .Shift_En(shift), .D(S), .Shift_Out(), .Data_Out());

    input logic [7:0] A, B,
    input logic fn,
    output logic[8:0] S
    ADD_SUB9 adder(.A(A), .B(B), .fn(fn), .S(ADDER_OUT));

    input logic CLR_XA

```

```

control control
(
    .CLR_LDB(NotClearA_LoadB),
    .Run(NotRun),
    .Reset(NotReset),
    .M(B[0]),
    .Clk(Clk),
    .CLR_XA_LD_B(CLR_XA_LD_B),
    .Shift_XAB(shift),
    .ADD(ADD),
    .SUB(SUB),
    .CLR_XA(CLR_XA)
);

HexDriver    HexAL (
    .In0(A[3:0]),
    .Out0(AhexL) );
HexDriver    HexBL (
    .In0(B[3:0]),
    .Out0(BhexL) );

//When you extend to 8-bits, you will need more HEX drivers to view upper nibble of registers, for now set to 0
HexDriver    HexAU (
    .In0(A[7:4]),
    .Out0(AhexU) );
HexDriver    HexBU (
    .In0(B[7:4]),
    .Out0(BhexU) );

endmodule

```

Module: lab5\_toplevel.sv

Inputs: [7:0] S, Clk, Reset, Run, ClearA\_LoadB

Outputs: logic[6:0] AhexU, AhexL, BhexU, BhexL,  
 logic[7:0] Aval, Bval,  
 logic X

Description: This module build a 8-bit Multiplier, with the modules shown below

Purpose: Top lever Module which aggregagates all the design modules.

```

1 module reg_8 (input logic Clk, Reset, Shift_In, Load, Shift_En,
2               input logic [7:0] D,
3               output logic Shift_Out,
4               output logic [7:0] Data_Out);
5
6     always_ff @ (posedge Clk)
7     begin
8         if (Reset) //notice, this is a synchrhonous reset, which is recommended on the FPGA
9             Data_Out <= 8'h0;
10        else if (Load)
11            Data_Out <= D;
12        else if (Shift_En)
13            begin
14                //concatenate shifted in data to the previous left-most 3 bits
15                //note this works because we are in always_ff procedure block
16                Data_Out <= { Shift_In, Data_Out[7:1] };
17            end
18        end
19
20    assign Shift_Out = Data_Out[0];
21
22 endmodule
23

```

Module: reg\_8

Inputs: [7:0] D, Clk, Reset, Shift\_In, Load, Shift\_En

Outputs: [7:0] Data\_out, Shift\_Out

Description: This is a positive-edge triggered 8-bit register with asynchronous reset and synchronous load. When Load is high, data is loaded from Din into the register on the positive edge of Clk.

Purpose: This module is used to create the registers that store operands A and B in the adder circuit.

```

1
2 // The 8-bit (or 9-bit) ripple adder with sign extension
3 module ADD_SUB9
4 (
5     input  logic[7:0]  A, B,
6     input  logic       fn,
7     output logic[8:0]  S
8 );
9
10
11 logic c0,c1,c2, c3, c4, c5, c6, c7; //internal carries in the 8-bit adder
12 logic [7:0] BB; //internal B or NOT(B)
13 logic A8, BB8; //internal sign extension bits
14
15
16 assign BB = (B ^ {8{fn}}); // when fn=1, complement B
17 assign A8 = A[7]; assign BB8 = BB[7]; // Sign extension bits
18 // copied from sign-bits
19
20 full_adder FA0(.x(A[0]), .y(BB[0]), .z(fn), .s(S[0]), .c(c0));
21 full_adder FA1(.x(A[1]), .y(BB[1]), .z(c0), .s(S[1]), .c(c1));
22 full_adder FA2(.x(A[2]), .y(BB[2]), .z(c1), .s(S[2]), .c(c2));
23 full_adder FA3(.x(A[3]), .y(BB[3]), .z(c2), .s(S[3]), .c(c3));
24 full_adder FA4(.x(A[4]), .y(BB[4]), .z(c3), .s(S[4]), .c(c4));
25 full_adder FA5(.x(A[5]), .y(BB[5]), .z(c4), .s(S[5]), .c(c5));
26 full_adder FA6(.x(A[6]), .y(BB[6]), .z(c5), .s(S[6]), .c(c6));
27 full_adder FA7(.x(A[7]), .y(BB[7]), .z(c6), .s(S[7]), .c(c7));
28 full_adder FA8(.x(A8), .y(BB8), .z(c7), .s(S[8]), .c(c));
29
30
31 endmodule
32
33

```

Module: ADD\_SUB9.sv

Inputs: [7:0] A, B; fn

Outputs: [8:0] S

Description: This is a 9-bit sign extension ripple Adder build by one-bit full adder. When fn is 1, the adder will perform  $A-B \rightarrow S$ , when fn is 0, the adder will perform  $A+B \rightarrow S$ .

Purpose: This module is used to compute the results of  $A+S$  or  $A-S$ ,  $S[7:0]$  will be loaded to A and  $S[8]$  will be loaded to X.

```

8
9 /* one-bit adder */
10 module full_adder (input x,y,z,
11                    output s,c );
12     assign s = x^y^z; // getting s at corresponding position
13     assign c = (x&y) | (y&z) | (x&z); // getting C_out
14
15 endmodule

```

Module: full\_adder

Inputs: x,y,z

Outputs: s,c

Description: one-bit full\_adder, compute  $x+y$  with carry in z.

Purpose: Basic build element for ADD\_SUB9

```

// D-flip flop for extend bit X
module Dreg (input Clk, Load, Reset, D,
            output logic Q );
    always_ff @ (posedge Clk)
    begin
        if (Reset)
            Q <= 1'b0;
        else if
            (Load) Q <= D;
        else //in most cases this is redundant, maintaining Q inferred
            Q <= Q;
    end
endmodule

```

Module: Dreg

Inputs: Clk, Load, Reset, D

Outputs: Q

Description: This is a positive-edge triggered 1-bit D-Flip-Flop with asynchronous reset and synchronous load. When Load is high, data is loaded from D into the register on the positive edge of Clk.

Purpose: Store the sign extension bit X.

```

1
2
3 module control
4   (
5     input logic CLR_LDB,
6     input logic Run,
7     input logic Reset,
8     input logic M,
9     input logic Clk,
10    output logic CLR_XA_LD_B,
11    output logic Shift_XAB,
12    output logic ADD, // ADD = 1 for add op
13    output logic SUB, // SUB = 1 for sub op
14    output logic CLR_XA
15  );
16
17  // have synthesis tool pick encoding (recommended)
18  enum logic [4:0] {S0, S1, S2, S3, S4, S5, S6, S7, S8, S9, S10, S11, S12, S13, S14, S15, S16} curr_state, next_state;
19
20  assign CLR_XA_LD_B = CLR_LDB;
21
22  always_ff @ (posedge Clk)
23  begin
24    if(Reset) // Synchronous Reset
25      curr_state <= S0; // Start state
26    else
27      curr_state <= next_state;
28  end
29

```

```

31 always_comb
32 begin
33     next_state = curr_state; //not all combinations accounted for below
34     unique case (curr_state)
35         // XA <- A + M * S
36         S0: begin
37             CLR_XA = 0;
38             if (Run == 1)
39                 begin
40                     Shift_XAB = 0;
41                     SUB = 0;
42                     if (M == 1)
43                         ADD = 1;
44                     else
45                         ADD = 0;
46                     next_state = S1;
47                 end
48             else
49                 begin
50                     Shift_XAB = 0;
51                     SUB = 0;
52                     ADD = 0;
53                     next_state = S0;
54                 end
55             end
56         // SHIFT XAB
57         S1: begin
58             CLR_XA = 0;
59             Shift_XAB = 1;
60             SUB = 0;
61             ADD = 0;
62             next_state = S2;
63         end
64         // XA <- A + M * S
65     endcase
66 end
67
68 // SHIFT XAB
69 S15: begin
70     CLR_XA = 0;
71     Shift_XAB = 1;
72     SUB = 0;
73     ADD = 0;
74     next_state = S16;
75 end
76 // wait until Run switch returns 0
77 S16: begin
78     Shift_XAB = 0;
79     SUB = 0;
80     ADD = 0;
81
82     if (Run==1)
83         begin
84             next_state = S16;
85             CLR_XA = 0;
86         end
87     else
88         begin
89             next_state = S0;
90             CLR_XA = 1;
91         end
92     end
93 end
94 endcase
95 end
96 endmodule

```

(Here I only show part of the states to reduce redundancy, there are 17 states in total, you can check the entire code in project file)

Module: control.sv

Inputs: CLR\_LDB, Run, Reset, M, Clk

Outputs: CLR\_XA\_LD\_B, Shift\_XAB, ADD, SUB, CLR\_XA

Description: The control module implement a state machine for the circuit control, there are 17 states in total, the state machine implement the "add-shift" algorithm and ensure Multiplication is only executed once.

Purpose: Provide control for the entire circuit.

```

1 module HexDriver (input logic [3:0] In0,
2                   output logic [6:0] Out0);
3
4     always_comb
5     begin
6         unique case (In0)
7             4'b0000 : Out0 = 7'b1000000; // '0'
8             4'b0001 : Out0 = 7'b1111001; // '1'
9             4'b0010 : Out0 = 7'b0100100; // '2'
10            4'b0011 : Out0 = 7'b0110000; // '3'
11            4'b0100 : Out0 = 7'b0011001; // '4'
12            4'b0101 : Out0 = 7'b0010010; // '5'
13            4'b0110 : Out0 = 7'b0000010; // '6'
14            4'b0111 : Out0 = 7'b1111000; // '7'
15            4'b1000 : Out0 = 7'b0000000; // '8'
16            4'b1001 : Out0 = 7'b0010000; // '9'
17            4'b1010 : Out0 = 7'b00001000; // 'A'
18            4'b1011 : Out0 = 7'b0000011; // 'b'
19            4'b1100 : Out0 = 7'b1000110; // 'C'
20            4'b1101 : Out0 = 7'b0100001; // 'd'
21            4'b1110 : Out0 = 7'b0000110; // 'E'
22            4'b1111 : Out0 = 7'b0001110; // 'F'
23            default : Out0 = 7'bx;
24        endcase
25    end
26 endmodule

```

Module: HexDriver


Inputs: [3:0] In0

Outputs: [6:0] Out0





Description: Input a value and Output a code for displaying corresponding Hex representation.



Purpose: To make the screen show the result of Multiplication in Hex Format.



**Block Diagram for each module:**

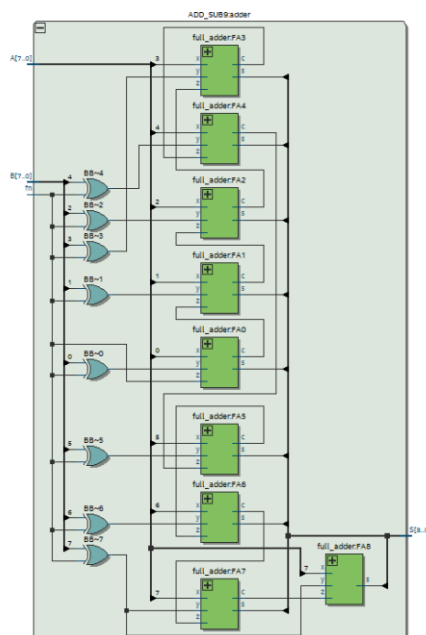



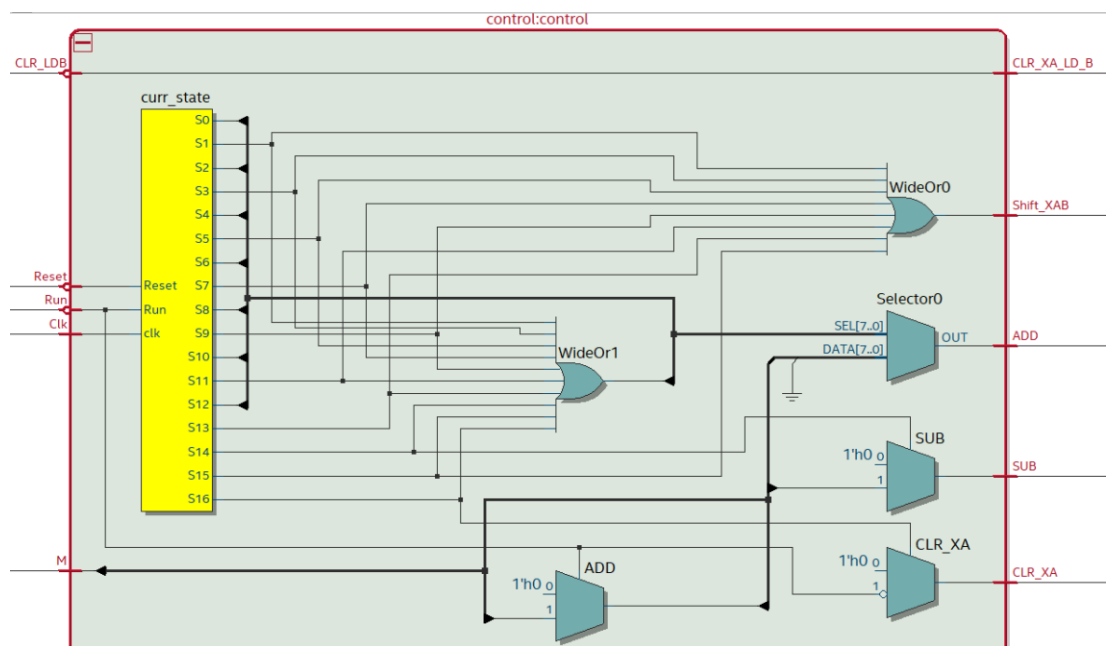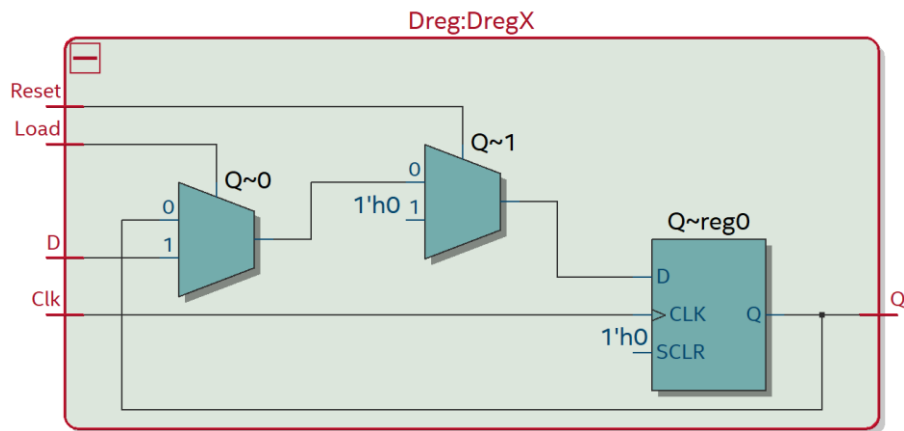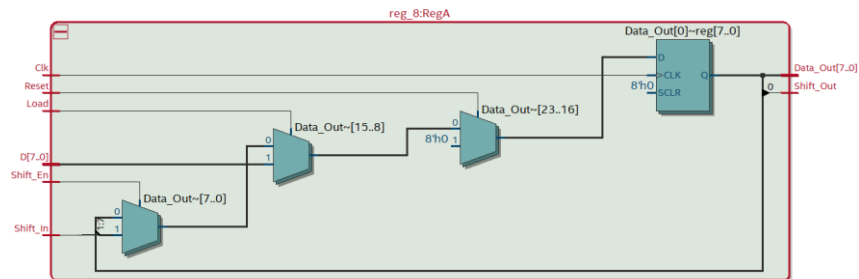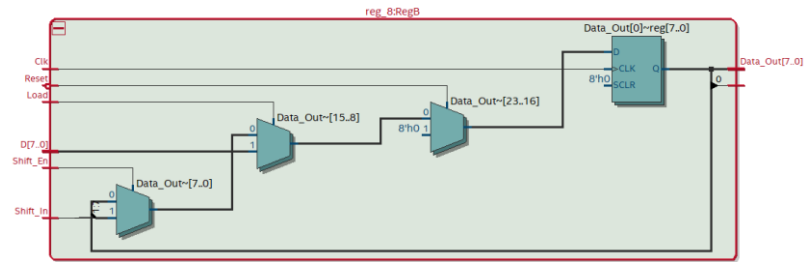


  

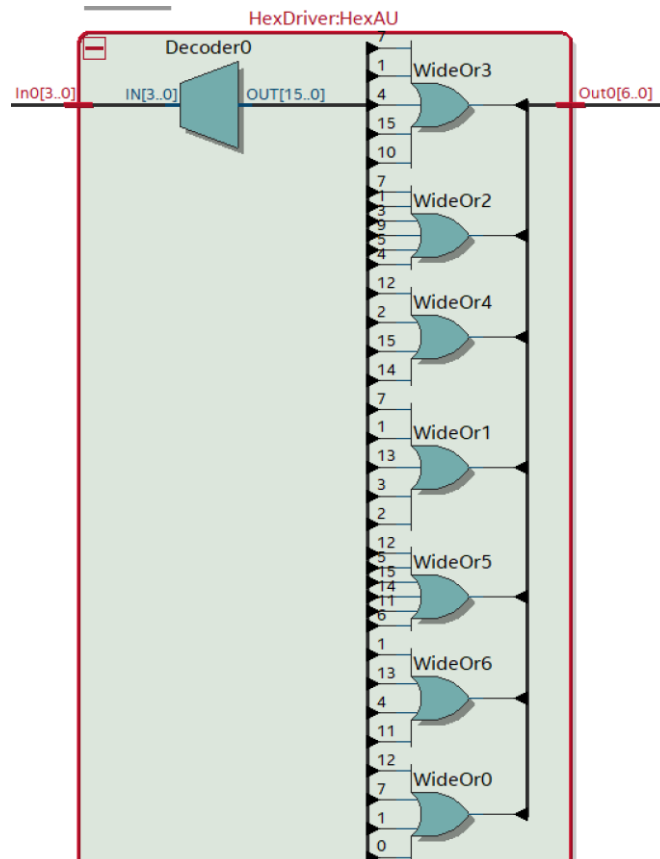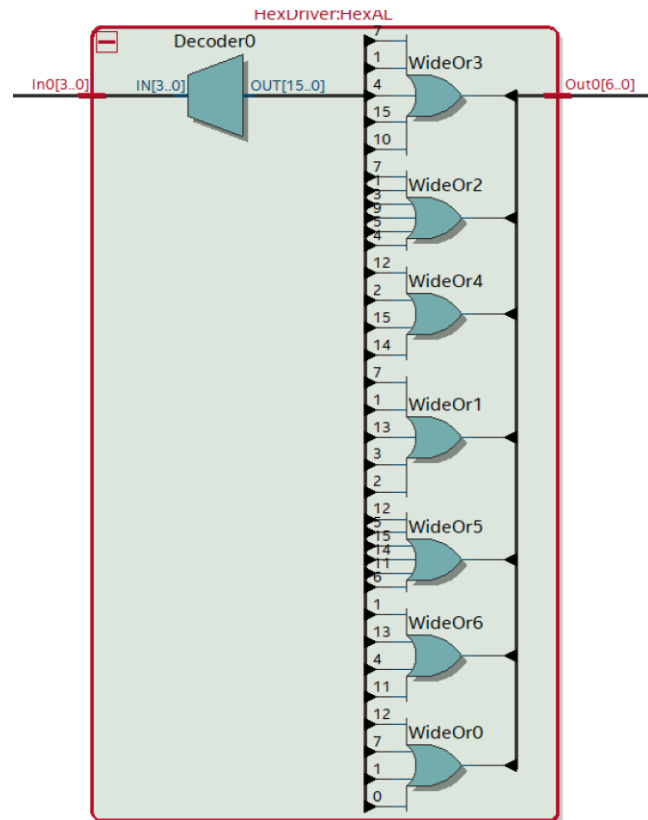


[illegible][illegible]

 
Single\_Run Execution(Test1:  $59 \times 7 = 413$ )




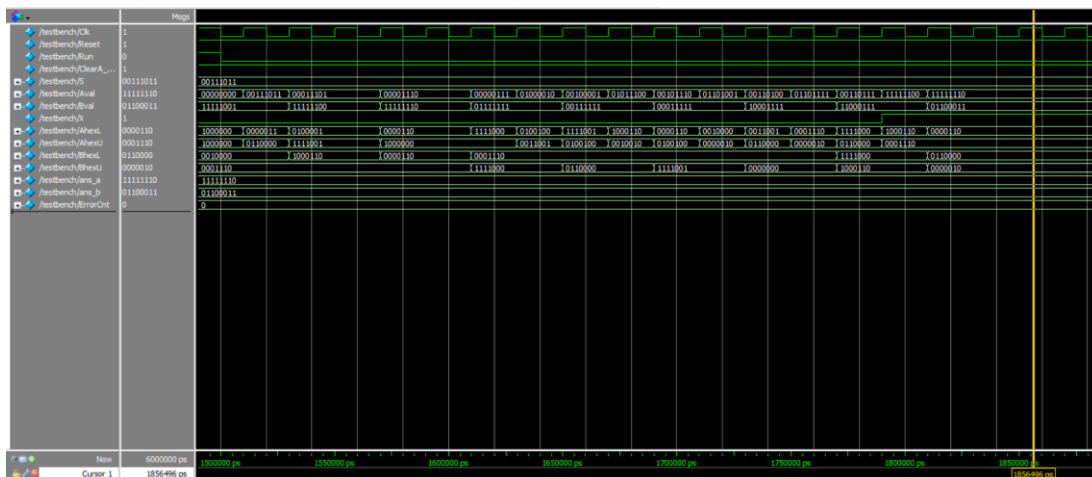Single\_Run Execution(Test2:  $-59 \times 7 = 413$ )



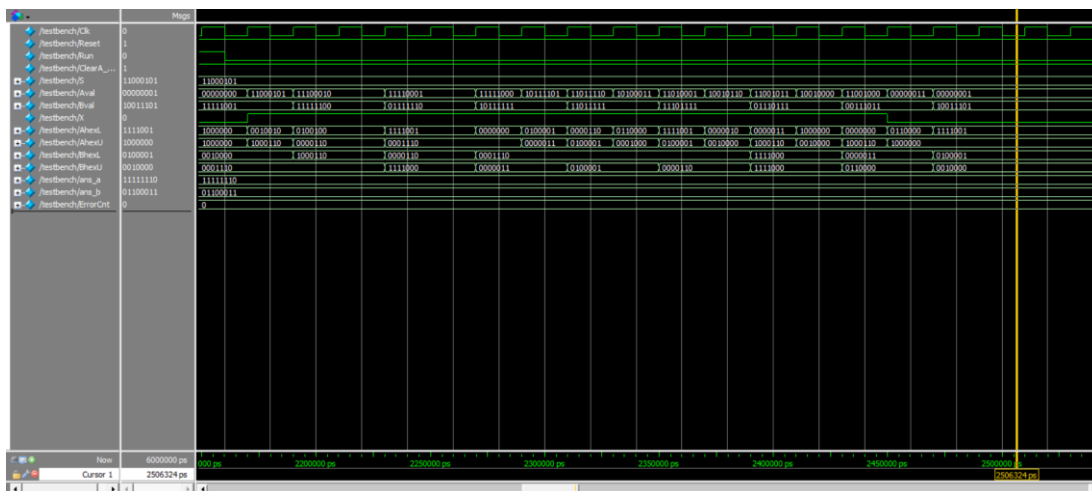Single\_Run Execution(Test3:  $59 \times -7 = -413$ )



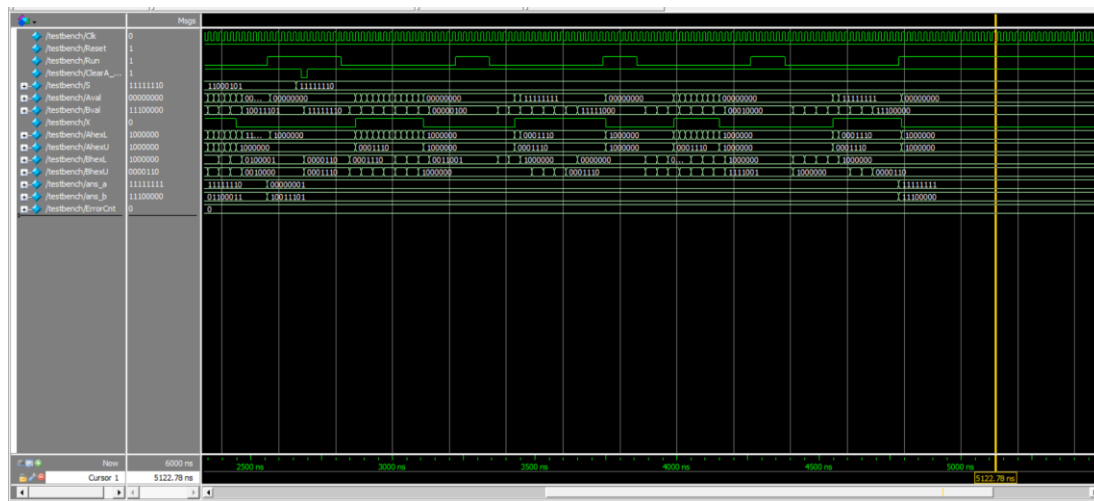

Consecutive Multiplication(Test5:  $-2*-2*-2*-2*-2 = -32$ )

## 5. Answers to post-lab questions

1.) Refer to the Design Resources and Statistics in IQT.30-32 and complete the following design statistics table.

LUT	89
DSP	0
Memory (BRAM)	0
Flip-Flop	51
Frequency	67.98Mhz
Static Power	98.51mW
Dynamic Power	3.97mW
Total Power	146.50mW

2)

### What is the purpose of the X register. When does the X register get set/cleared?

The X register is used to store the sign bit of value in the register A, which will produce the extended bit to register A during the shift operations. X will get cleared when Reset button or ClearA\_LoadB button is pressed, or when FSM translate from terminated state (S16) to start

state (S0) once Run=0 (button Run released) detected in terminated state (Note: the setting allows to perform Consecutive Multiplication as requested).

**What are the limitations of continuous multiplications? Under what circumstances will the implemented algorithm fail?**

The valid range of multiplications is limited, since the register X and A will be cleared after each multiplication and the result should be contained into the register B. The continuous multiplications will cause overflow when the expected result (during the multiplications) runs out of range -- (-128, 127) for 8-bit 2's complement, that is, at the beginning of next multiplication, the bits over [15:8] will be lost in this case.

**What are the advantages (and disadvantages?) of the implemented multiplication algorithm over the pencil-and-paper method discussed in the introduction?**

Compared with pencil-and-paper method, the implemented multiplication algorithm helps save the memory space, that is, using only three 8-bit registers and one DFF in the implementation instead of memorizing all values of each step. However, the valid range of consecutive multiplication of this algorithm is quite limited, since the output of each multiplication (except the final result) is limited in 8-bit 2's Complement within (-128,127), which could simply cause overflow by the multiplications of two 8-bit inputs.

## **6. Conclusion**

**Discuss functionality of your design. If parts of your design didn't work, discuss what could be done to fix it**

We passed all the five given tests, I think our circuits can perform all the basic 8-bit multiplication functionality as required. However, our design can be further improved to decrease the latency, that is we can skip the add state if M=0.

**Was there anything ambiguous, incorrect, or unnecessarily difficult in the lab manual or given materials which can be improved for next semester? You can also specify what we did right so it doesn't get changed.**

Run, Reset and ClearA\_LoadB are inverted on the given testbench, however we didn't find any declaration on the lab manual, which is quite confusing and takes us some time to figure it out.